

# Contents

*Preface*

v

<b>1. Fundamentals of Electrical Engineering—Circuit Theory Concepts</b>	<b>1–34</b>
1.1 Introduction 1	
1.1.1 Electric Charge and Electric Current 1	
1.1.2 Direction of Current 2	
1.1.3 Coulomb’s Law 3	
1.2 Electromotive Force and Potential Difference 3	
1.3 Ohm’s Laws 5	
1.4 Basic Parameters of Circuit (R–L–C) 6	
1.4.1 Resistance 6	
1.4.2 Inductance 9	
1.4.3 Capacitance 12	
1.4.4 Capacitance in Series 13	
1.4.5 Capacitors in Parallel 14	
1.4.6 Capacitance of a Parallel Plate Capacitor 14	
1.4.7 Capacitance of Concentric Spheres 15	
1.4.8 Capacitance of Two Coaxial Cylinders 16	
1.5 Electromagnetic Induction 17	
1.6 Laws of Electromagnetic Induction 17	
1.7 Kirchhoff’s Laws 18	
1.8 Ampere’s Law 19	
1.9 Sources 20	
1.9.1 Source Transformation 21	
<b>2. Electrical Circuit Analysis</b>	<b>35–94</b>
2.1 Circuit Concepts 35	
2.1.1 Concept of Network/Circuit 35	
2.2 Network Terminology 35	
2.3 Classification of Electrical Networks 37	
2.4 Basic Circuit Elements 38	
2.5 Energy Sources 39	
2.6 Current Division Rule 41	
2.7 Voltage Division Rule 41	
2.8 Source Transformation 41	
2.8.1 Transformation of Voltage Source to Current Source 42	
2.8.2 Transformation of Current Source to Voltage Source 42	

2.9 Kirchhoff's Law's	46
2.9.1 Kirchhoff's Current Law (KCL) or First Law	46
2.9.2 Kirchhoff's Voltage Law (KVL) or Second Law	47
2.10 Loop Analysis or Mesh Analysis	47
2.11 Nodal Analysis	49
2.12 Star-delta Transformation	51
2.12.1 Network Reduction By Delta-Star and Star-Delta Transformation	52
<b>3. AC Fundamentals</b>	<b>95–127</b>
3.1 Introduction	95
3.1.1 AC Quantity	95
3.2 Types of AC Waveforms	95
3.3 Advantages of Sinusoidal Waveforms	96
3.4 Generation of Alternating Quantity	96
3.4.1 Equations of the Alternating Voltages and Currents	97
3.5 Important Definitions Related to AC Quantity	98
3.6 Important Values of Alternating Quantities	101
3.7 Root Mean Square (RMS) or Effective Values, Average Value, Form-Factor and Peak Factor of Alternating Current and Alternating Voltage for Sinusoidal Waveform	101
3.8 RMS Value or Effective Value, Form Factor for Half-wave Voltage and Current	104
3.9 RMS Value, Average Value, Form Factor and Peak Factor for Square Wave of Voltage and Current	105
3.10 RMS Value, Average Value, Form Factor, Peak Factor of Triangular Wave for Current and Voltage	106
3.11 Concept of Phasor	109
3.11.1 Phasor Diagram Using RMS Values	110
3.11.2 Phase and Phase Angle	110
3.11.3 Phase Difference	110
3.11.4 Conventions for Drawing Phasor Diagrams	112
3.12 Addition and Subtraction of Alternating Quantities	113
<b>4. Steady State Analysis of Single Phase AC Circuits</b>	<b>128–194</b>
4.1 Introduction	128
4.2 AC Circuit	128
4.2.1 AC Circuit Containing Pure Resistor Only	128
4.2.2 AC Circuit Containing Pure Inductor Only	131
4.2.3 AC Circuit Containing Pure Capacitance Only	133
4.3 AC Series Circuit	136
4.3.1 AC Circuit Containing Resistance and Inductance in Series	136
4.3.2 Apparent Power, Real Power and Reactive Power	139
4.3.3 AC Circuit Containing Resistance and Capacitance in Series	140
4.4 AC Circuit Containing Resistance, Inductance and Capacitance in Series (R-L-C Series)	144
4.4.1 Impedance Triangle	145
4.4.2 Power and Power Triangle	146
4.5 AC Parallel Circuit	147
4.6 Method of Solving AC Parallel Circuit	148
4.6.1 By Phasor Diagram Method	148
4.6.2 By Phasor Algebra	149

---

4.6.3 Impedance Method	150
4.6.4 Admittance Method	151
4.7 Resonance in R-L-C Circuits	154
4.7.1 Introduction	154
4.7.2 Series or Voltage Resonance	155
4.7.3 Graphical Representation of Resonance in An R-L-C Series Circuits	156
4.7.4 Resonance Curve	156
4.7.5 Determination of Bandwidth and Edge Frequencies	157
4.7.6 Quality Factor of a Series Resonant Circuit	158
4.7.7 Parallel or Current Resonance	159
4.7.8 Q-factor or Current Magnification Factor for Parallel Resonance Circuit	161
<b>5. DC Network Theorems</b>	<b>195–272</b>
5.1 Introduction	195
5.2 Superposition Theorem	195
5.2.1 Steps to Solve Problems on Superposition Theorem	195
5.3 Thevenin's Theorem	199
5.3.1 Steps for Solving Problems	200
5.3.2 Applications	201
5.3.3 Advantages	201
5.3.4 Disadvantages	201
5.4 Norton's Theorem	207
5.4.1 Steps for Solving Problems on Norton's Theorem	207
5.5 Maximum Power Transfer Theorem	211
5.5.1 Proof of Maximum Power Transfer Theorem	211
5.5.2 Steps for Solving Problems on Maximum Power Transfer Theorems	212
5.6 Reciprocity Theorem	212
<b>6. AC Network Theorems</b>	<b>273–316</b>
6.1 Introduction	273
6.2 Star-Delta and Delta-Star Transformations	273
6.2.1 Delta to Star Conversion	274
6.2.2 Star to Delta Conversion	275
6.3 Source Transformations	275
6.4 Network Terminology	277
6.4.1 Loop and Mesh	277
6.4.2 Node and Junction	277
6.4.3 Sign Convension	277
6.5 Kirchhoff's Laws	277
6.5.1 Super-Node Analysis	278
6.5.2 Super-Mesh Analysis	279
6.6 Superposition Theorem	280
6.6.1 Applications of Superposition Theorem	280
6.6.2 Limitations of Superposition Theorem	280
6.7 Thevenin's and Norton's Theorems	280
6.7.1 Procedure to Obtain $V_{th}$ and $Z_{th}$ or $I_N$ and $Z_n$	281
6.7.2 Applications of Thevenin's and Norton's Theorems	282
6.7.3 Limitations	282
6.7.4 Application of Millman's Theorem	285
6.7.5 Limitations of Milliman's Theorem	285
6.8 Maximum Power Transfer Theorem	285

<b>7. Three Phase AC Circuit</b>	<b>317–341</b>
7.1 Introduction	317
7.2 Three Phase Electric System	317
7.2.1 Comparison of Single Phase and Three Phase Systems	318
7.3 Balanced or Unbalanced Load	318
7.4 Generation of 3- $\phi$ EMFs	319
7.5 Phase Voltage, Phase Current, Line Voltage and Line Current	319
7.6 Star (Y) Connected System	320
7.6.1 Power in 3- $\phi$ AC System	320
7.7 Delta ( $\Delta$ ) Connection System	321
7.8 Measurement of Power in 3- $\phi$ AC Circuit	322
7.8.1 One Wattmeter Method	322
7.8.2 Two Wattmeter Method	322
7.8.3 Three Wattmeter Method	326
<b>8. Transients</b>	<b>342–358</b>
8.1 Introduction	342
8.2 Types of Transients	342
8.3 Important Differential Equations	343
8.4 Transients in R-L Circuit (DC)	344
8.5 Short Circuit Current	346
8.6 Time Constant	347
8.7 Transients in R-L Circuits (AC)	347
8.8 Transients in R-C Series Circuits (DC)	349
8.9 Transients in R-C Series Circuits (AC)	351
8.10 Double Energy Transients	352
<b>9. Measuring Instruments</b>	<b>359–371</b>
9.1 Introduction	359
9.2 Classification	359
9.3 Operation of Indicating Instruments	360
9.4 Types of Measuring Instruments	360
9.4.1 Permanent Magnet Moving Coil Instrument (PMMC)	361
9.4.2 Dynamometer Type Instrument	363
9.4.3 Dynamometer Type Wattmeter	363
9.5 Extension of Range of Moving Coil Instrument	365
9.6 Moving Iron Instrument	367
<b>10. Magnetic Circuits</b>	<b>372–392</b>
10.1 Introduction	372
10.2 Magnetic Circuit Concept	372
10.3 Magnetic Circuit with DC Excitations	375
10.4 Analogy between Electric and Magnetic Circuits	377
10.5 Magnetic Circuit Calculation	379
10.6 Electromagnetism	379
10.7 Nature of Induced EMF	380
10.7.1 Magnetic Leakage and Fringing	381
<b>11. Single Phase Transformer</b>	<b>393–430</b>
11.1 Introduction	393
11.2 Transformer as a Device	393

- 11.3 Classification of Transformer 394
- 11.4 Principle of Operation of Transformer 395
- 11.5 EMF Equation of Transformer 396
- 11.6 Transformation Ratio (K) 397
- 11.7 Ideal Transformer 398
- 11.8 Practical Transformer 398
- 11.9 Practical Transformer on No-Load 399
- 11.10 Transformer on Load 399
- 11.11 Equivalent Circuit Diagram 402
- 11.12 Losses in Transformer 405
- 11.13 Transformer Efficiency 407
  - 11.13.1 Condition for Maximum Power Efficiency 408
  - 11.13.2 Voltage Regulation of a Transformer 408
  - 11.13.3 Efficiency from Transformer Tests 410
  - 11.13.4 Calculation of Efficiency from OC and SC Test 411
- 11.14 Auto Transformer 412

## 12. DC Machines

431–460

- 12.1 Introduction 431
- 12.2 Concept of Electro-Mechanical Energy Conversion 431
- 12.3 Types of DC Machines 431
  - 12.3.1 Separately Excited DC Machine 432
  - 12.3.2 Self Excited DC Machine 432
- 12.4 Construction of DC Machine 434
  - 12.4.1 Yoke 435
  - 12.4.2 Pole Core and Pole Shoes 435
  - 12.4.3 Field Coils 435
  - 12.4.4 Armature Core 436
  - 12.4.5 Armature Winding 437
  - 12.4.6 Commutator 437
  - 12.4.7 Brush Assembly and Brush Gear 437
  - 12.4.8 Bearings 437
- 12.5 Working of DC Generator 437
- 12.6 EMF Equation of DC Generator 439
- 12.7 Important Relations for Various Types of DC Generators 441
  - 12.7.1 Separately Excited DC Generator 441
  - 12.7.2 Shunt Wound DC Generator 442
  - 12.7.3 Series Wound DC Generator 442
  - 12.7.4 Compound Wound DC Generator 443
- 12.8 Working Principle of DC Motor 446
  - 12.8.1 Significance of Back EMF in DC Motor 446
  - 12.8.2 Important Relations for Different Types of DC Motors 447
- 12.9 Torque Developed in a Motor 451
- 12.10 Characteristics of DC Motors 453
  - 12.10.1 Characteristics of DC Shunt Motor 453
  - 12.10.2 Characteristics of DC Series Motor 454
  - 12.10.3 Characteristics of DC Compound Motors 455

<b>13. Induction Motors</b>	<b>461–483</b>
13.1 Three Phase Induction Motor	461
13.2 Construction of 3- $\phi$ Induction Motor	462
13.3 Operation of 3- $\phi$ Induction Motor	462
13.4 Slip Speed, Slip, Synchronous Speed	463
13.4.1 Rotor Frequency ( $f_r$ )	463
13.4.2 Rotor Current, Rotor Power Factor	463
13.5 Power Stages in 3- $\phi$ Induction Motor	464
13.6 Electromagnetic Torque Expression for 3- $\phi$ Induction Motor	465
13.7 Torque Slip and Torque-Speed Characteristics of 3- $\phi$ Induction Motor	465
13.8 Need of a Starter for 3- $\phi$ Induction Motor and Starting Method of 3- $\phi$ Induction Motor	466
13.8.1 DOL (Direct Online Starter)	467
13.8.2 Reduced Voltage Starting	467
13.8.3 Auto-Transformer Starting	468
13.8.4 Star-Delta Method of Starting	468
13.9 Some Important Formulae	469
13.10 Single Phase Induction Motor	476
13.11 Construction of a Single Phase Induction Motor	476
13.12 Working Principle of Single Phase Induction Motor	476
13.13 Why Single Phase Induction Motor is not Self-Starting	477
13.13.1 Double Revolving Field Theory	477
13.13.2 Single Phase Induction Motor is Self-Starting	478
13.14 Types of Single Phase Induction Motor or Phase Splitting Method of Starting	478
13.14.1 Split Phase Induction Motor	479
13.14.2 Capacitor Start Induction Motor	480
13.14.3 Capacitor Start Capacitor Run Motor	480
13.14.4 Shaded Pole Motor	482
<b>14. Three Phase Synchronous Machines</b>	<b>484–490</b>
14.1 Introduction	484
14.2 Construction of an Alternator	484
14.3 Principle of Operation of an Alternator	485
14.4 Frequency of Induced EMF	486
14.5 Synchronous Motor	487
14.6 Operating Principle	487
14.7 Method of Starting a Synchronous Motor	489
14.8 V-Curves	489
14.9 Application of Three Phase Synchronous Motor	489
14.10 Disadvantages of Synchronous Motors	489
<b>Index</b>	<b>491–492</b>